

VHDL ASSIGNMENT: 1:8 DEMUX

Name: Shreya Mamadapur

Student ID: C0774035

Source code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity DeMUX_onetoeight is
    Port ( I: in  STD_LOGIC; --1 input pin
          S: in  STD_LOGIC_vector( 2 downto 0); --3 select pins required for 8 DEMUX outputs
          STRB_n : in  STD_LOGIC; -- active low enable pin
          O : out STD_LOGIC_vector( 7 downto 0)); --8 output pins
end DeMUX_onetoeight;

architecture Behavioral of DeMUX_onetoeight is
begin
    process(STRB_n,S,I)
    begin
        if STRB_n = '0' then -- chip is enabled only when STROBE is low
            O <= (others => '0'); -- all other pins except the selected output must be low
            if S = "000" then -- output pin O(0) is selected
                O(0) <= I; -- O(0) will follow the value in input pin
            elsif S = "001" then
                O(1) <= I;
            elsif S = "010" then
                O(2) <= I;
            elsif S = "011" then
                O(3) <= I;
            elsif S = "100" then
                O(4) <= I;
            elsif S = "101" then
                O(5) <= I;
            elsif S = "110" then
                O(6) <= I;
            elsif S = "111" then
                O(7) <= I; -- O(7) will follow the value in input pin
            end if;
        end if;
    end process;
end Behavioral;
```

VHDL ASSIGNMENT: 1:8 DEMUX

Waveform editor:

Select pin S = 101 i.e O(5) is selected.

So, O(5) follows input I, whenever strb_n is low.

All other outputs are low.

